

# Assignment 1

## Digital Design Verification

### Contents

<b>1</b>	<b>Priority Encoder</b>	<b>2</b>
1.1	1. Design	2
1.2	2. Verification Plan	2
1.3	3. Testbench	2
1.4	4. Do File	4
1.5	5. Coverage Report	4
<b>2</b>	<b>ALU 4-bit</b>	<b>5</b>
2.1	1. Design	5
2.2	2. Verification Plan	6
2.3	3. Testbench	6
2.4	4. Do File	8
2.5	5. Coverage Report	8
<b>3</b>	<b>DSP</b>	<b>9</b>
3.1	1 Design	9
3.2	Bug Fixes	10
3.3	2. Verification Plan	10
3.4	3 Testbench	10
3.5	4 Do File	13
3.6	5 Coverage Report	13

1 Priority Encoder

1.1 1. Design

```
1 // Bug fix: Compilation error due to 'Y' not being defined as a reg type resolved by adding 'reg' to the Y declaration.
2 // Bug fix: 'valid' output was not reset to zero when synchronous reset was asserted resolved by adding a reset condition for 'valid'
  in the always block.
3 module priority_enc (
4     input  clk,
5     input  rst,
6     input  [3:0] D,
7     output reg [1:0] Y, // Defined as 'reg' to hold value in always block
8     output reg valid    // Ensured proper reset behavior
9 );
10
11 always @(posedge clk) begin
12     if (rst) begin
13         Y <= 2'b0; // Reset Y to 0 on reset
14         valid <= 1'b0; // Reset valid to 0 on reset
15     end else begin
16         casex (D)
17             4'b1000: Y <= 0;
18             4'bX100: Y <= 1;
19             4'bXX10: Y <= 2;
20             4'bXXX1: Y <= 3;
21         endcase
22         valid <= (~|D) ? 1'b0 : 1'b1; // Set valid based on D input
23     end
24 end
25
26 endmodule
```

1.2 2. Verification Plan

Label	Design Re-quirement De- scription	Stimulus Generation	Functional Coverage	Functionality Check
RESET_TEST	When reset is asserted, out-put Y should be 00 and valid should be 0	Directed at the start of the simulation	-	A checker in the testbench verifies Y = 00 and valid = 0
ALL_ZERO	When D is 0000, output Y should be un-defined (xx) and valid should be 0	Directed test with D = 0000	-	A checker in the testbench verifies Y = xx and valid = 0
PRIORITY_0	When D is 1000, Y should be 00 and valid should be 1	Directed test with D = 1000	-	A checker in the testbench verifies Y = 00 and valid = 1
PRIORITY_1	When the high-est priority bit is at 01 (D = 1100 or 0100), Y should be 01	Directed tests with D = 1100, 0100	-	A checker in the testbench verifies Y = 01 and valid = 1
PRIORITY_2	When the high-est priority bit is at 10 (D = 0010, 0110, etc.), Y should be 10	Directed tests with D = 0010, 0110...	-	A checker in the testbench verifies Y = 10 and valid = 1
PRIORITY_3	When the high-est priority bit is at 11 (D = 0001, 0011, etc.), Y should be 11	Directed tests with D = 0001, 0011...	-	A checker in the testbench verifies Y = 11 and valid = 1

Table 1: Verification Plan

1.3 3. Testbench

```
1 `timescale 1ns/1ps
2 module priority_enc_tb();
3
4     //-----
5     //----- TB signal declaration -----
6     //-----
7     logic  clk;
8     logic  rst; // note : active high synchronous reset
9     logic  [3:0] D;
10    logic  [1:0] Y;
11    logic  valid;
12
13    int error_count = 0; // Error count variable
14
15    //-----
16    //----- instantiate DUT -----
17    //-----
18    priority_enc DUT (
19        .clk(clk),
20        .rst(rst),
21        .D(D),
22        .Y(Y),
23        .valid(valid)
24    );
25
26    //-----
27    //----- generate clock -----
28    //-----
29    localparam CLOCK_PERIOD = 10;
30    always begin
31        #(CLOCK_PERIOD/2) clk = ~clk;
32    end
33
34    //-----
35    //----- reset task -----
36    //-----
37    task check_rst(input [1:0] expected_output);
38    begin
39        @(negedge clk);
40        if(Y != expected_output || valid != 1'b0) begin // using -- or not and --- as no one from two checking condition not be violated
41            error_count++;
42            $display("Reset test failed: rst=%0b, D=%0b, Y=%0b, valid=%0b, error count=%0d, time=%0t", rst, D, Y, valid, error_count, $time);
43            $stop;
44        end else begin
```

```

45         $display("Reset␣test␣passed:␣rst=%0b,␣D=%0b,␣Y=%0b,␣valid=%0b,␣time=%0t", rst, D, Y, valid, $time);
46         // wait 5ns then toggle reset
47         #(CLOCK_PERIOD/2) rst = 0;
48     end
49 end
50 endtask
51
52 //-----
53 //----- all zero task -----
54 //-----
55 task all_zero(input [1:0] expected_output);
56 begin
57     @(negedge clk);
58     if(Y != expected_output || valid != 1'b0) begin
59         error_count++;
60         $display("all_zero␣test␣failed:␣rst=%0b,␣D=%0b,␣Y=%0b,␣valid=%0b,␣error␣count=%0d,␣time=%0t", rst, D, Y, valid, error_count,
61             $time);
62         $stop;
63     end else begin
64         $display("all_zero␣test␣passed:␣rst=%0b,␣D=%0b,␣Y=%0b,␣valid=%0b,␣time=%0t", rst, D, Y, valid, $time);
65         #(CLOCK_PERIOD/2);
66     end
67 end
68 endtask
69
70 //-----
71 //----- check task -----
72 //-----
73 task check_fun(input [1:0] expected_output);
74 begin
75     @(negedge clk);
76     if(Y != expected_output || valid != 1'b1) begin
77         error_count++;
78         $display("check␣test␣failed:␣rst=%0b,␣D=%0b,␣Y=%0b,␣valid=%0b,␣error␣count=%0d,␣time=%0t", rst, D, Y, valid, error_count,
79             $time);
80         $stop;
81     end else begin
82         $display("check␣test␣passed:␣rst=%0b,␣D=%0b,␣Y=%0b,␣valid=%0b,␣time=%0t", rst, D, Y, valid, $time);
83         #(CLOCK_PERIOD/2);
84     end
85 end
86 endtask
87
88 //-----
89 //----- initial clock -----
90 //-----
91 initial begin
92     // initial values
93     clk = 1;
94     rst = 0;
95     D = 4'b1111;
96
97     //-----
98     // test case 1 : test reset
99     //-----
100     #CLOCK_PERIOD;
101     rst = 1 ;
102     check_rst(2'b00); // expected output is 00
103
104     //-----
105     // test case 1 : all zeros
106     //-----
107     D = 4'b0000;
108     all_zero(2'bxx);
109
110     //-----
111     // test case 2 : priority 0
112     //-----
113     D = 4'b1000;
114     check_fun(2'b00);
115
116     //-----
117     // test case 3 : priority 1
118     //-----
119     D = 4'b1100;
120     check_fun(2'b01);
121     D = 4'b0100;
122     check_fun(2'b01);
123
124     //-----
125     // test case 4 : priority 2
126     //-----
127     D = 4'b0010;
128     check_fun(2'b10);
129     D = 4'b0110;
130     check_fun(2'b10);
131     D = 4'b1010;
132     check_fun(2'b10);
133     D = 4'b1110;
134     check_fun(2'b10);
135
136     //-----
137     // test case 5 : priority 3
138     //-----
139     D = 4'b0001;
140     check_fun(2'b11);
141     D = 4'b0011;
142     check_fun(2'b11);
143     D = 4'b0101;

```

```
143     check_fun(2'b11);
144     D = 4'b0111;
145     check_fun(2'b11);
146     D = 4'b1001;
147     check_fun(2'b11);
148     D = 4'b1011;
149     check_fun(2'b11);
150     D = 4'b1101;
151     check_fun(2'b11);
152     D = 4'b1111;
153     check_fun(2'b11);
154
155     //-----
156     // finish simulation
157     //-----
158     #CLOCK_PERIOD;
159     $finish;
160     end
161
162 endmodule
```

 


Figure 1: simulation waveform

```
Transcript
VSIM 147> restart
# ** Note: (vsim-8009) Loading existing optimized design _opt2
# Loading sv_std.std
# Loading work.priority_enc_tb(fast)
# Loading work.priority_enc(fast)
VSIM 148> run -all
# Reset test passed: rst=1, D=1111, Y=0, valid=0, time=15000
# all_zero test passed: rst=0, D=0, Y=0, valid=0, time=25000
# check test passed: rst=0, D=1000, Y=0, valid=1, time=35000
# check test passed: rst=0, D=1100, Y=1, valid=1, time=45000
# check test passed: rst=0, D=100, Y=1, valid=1, time=55000
# check test passed: rst=0, D=10, Y=10, valid=1, time=65000
# check test passed: rst=0, D=110, Y=10, valid=1, time=75000
# check test passed: rst=0, D=1010, Y=10, valid=1, time=85000
# check test passed: rst=0, D=1110, Y=10, valid=1, time=95000
# check test passed: rst=0, D=1, Y=11, valid=1, time=105000
# check test passed: rst=0, D=11, Y=11, valid=1, time=115000
# check test passed: rst=0, D=101, Y=11, valid=1, time=125000
# check test passed: rst=0, D=111, Y=11, valid=1, time=135000
# check test passed: rst=0, D=1001, Y=11, valid=1, time=145000
# check test passed: rst=0, D=1011, Y=11, valid=1, time=155000
# check test passed: rst=0, D=1101, Y=11, valid=1, time=165000
# check test passed: rst=0, D=1111, Y=11, valid=1, time=175000
# ** Note: $finish      : priority_enc_tb.sv(159)
# Time: 190 ns  Iteration: 0  Instance: /priority_enc_tb
# 1
# Break in Module priority_enc_tb at priority_enc_tb.sv line 159
```

Figure 2: Transcript : all test cases passed

1.4 4. Do File

```
vlib work
vlog priority_enc.sv priority_enc_tb.sv +cover -covercells
vsim -voptargs=+acc work.priority_enc_tb -cover
add wave *
coverage save priority_enc_tb.ucdb -du priority_enc -onexit
run -all
```

1.5 5. Coverage Report

Coverage Report by instance with details

== Instance: /\priority_enc_tb#DUT			
== Design Unit: work.priority_enc			
Branch Coverage:			
Enabled Coverage	Bins	Hits	Misses Coverage
Branches	7	7	0 100.00%
=====Branch Details=====			
Branch Coverage for instance /\priority_enc_tb#DUT			
Line	Item	Count	Source

File	priority_enc.sv	IF Branch		
10		18	Count coming in to IF	
10	1	1	if (rst) begin	
13	1	17	end else begin	

Branch totals: 2 hits of 2 branches = 100.00%

CASE Branch				
14		17	Count coming in to CASE	
15	1	1	4'b1000: Y <= 0;	
16	1	2	4'bX100: Y <= 1;	
17	1	4	4'bXX10: Y <= 2;	
18	1	9	4'bXXX1: Y <= 3;	
		1	All False Count	

Branch totals: 5 hits of 5 branches = 100.00%

Statement Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Statements	8	8	0	100.00%

Statement Details

Statement Coverage for instance /\priority\_enc\_tb#DUT —

Line	Item	Count	Source
File	priority_enc.sv		
1			module priority_enc (
2			input clk ,
3			input rst ,
4			input [3:0] D,
5			output reg [1:0] Y,
6			output reg valid
7			);
8			
9	1	18	always @(posedge clk) begin
10			if (rst) begin
11	1	1	Y <= 2'b0;
12	1	1	valid <= 1'b0;
13			end else begin
14			casex (D)
15	1	1	4'b1000: Y <= 0;
16	1	2	4'bX100: Y <= 1;
17	1	4	4'bXX10: Y <= 2;
18	1	9	4'bXXX1: Y <= 3;
19			endcase
20	1	17	valid <= (~ D)? 1'b0: 1'b1;

Toggle Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Toggles	18	18	0	100.00%

Toggle Details

Toggle Coverage for instance /\priority\_enc\_tb#DUT —

	Node	1H->0L	0L->1H	" Coverage"
	D[0-3]	1	1	100.00
	Y[1-0]	1	1	100.00
	clk	1	1	100.00
	rst	1	1	100.00
	valid	1	1	100.00

Total Node Count = 9  
Toggled Node Count = 9  
Untoggled Node Count = 0

Toggle Coverage = 100.00% (18 of 18 bins)

Total Coverage By Instance (filtered view): 100.00%

## 2 ALU 4-bit

### 2.1 1. Design

```

1 // no bugs
2 module ALU_4_bit (
3     input  clk,
4     input  reset,
5     input  [1:0] Opcode,    // The opcode

```

```
6   input  signed [3:0] A,    // Input data A in 2's complement
7   input  signed [3:0] B,    // Input data B in 2's complement
8   output reg signed [4:0] C // ALU output in 2's complement
9 );
10
11 reg signed [4:0]      Alu_out; // ALU output in 2's complement
12
13 localparam            Add          = 2'b00; // A + B
14 localparam            Sub          = 2'b01; // A - B
15 localparam            Not_A        = 2'b10; // ~A
16 localparam            ReductionOR_B = 2'b11; // |B
17
18 // Do the operation
19 always @* begin
20     case (Opcode)
21         Add:           Alu_out = A + B;
22         Sub:           Alu_out = A - B;
23         Not_A:         Alu_out = ~A;
24         ReductionOR_B: Alu_out = |B;
25         default:       Alu_out = 5'b0;
26     endcase
27 end // always @ *
28
29 // Register output C
30 always @(posedge clk or posedge reset) begin
31     if (reset)
32         C <= 5'b0;
33     else
34         C<= Alu_out;
35 end
36
37 endmodule
```

2.2 2. Verification Plan

Label	Design Requirement Description	Stimulus Generation	Functional Coverage	Functionality Check
RESET.TEST	When the reset is asserted, the ALU's output (C) must initialize to 0	Drive reset high for one clock cycle (with defined A, B, Opcode) then de-assert it; check output immediately after clock edge	Reset behavior; Initialization	Compare C to expected value (5'b0) after reset is applied
ADDITION	With Opcode = 00, the ALU shall perform signed addition (A + B) with proper handling of negative values and potential overflow	Set Opcode to 2'b00 and apply multiple input vectors (e.g., 0+0, -1+(-1), 3+1, -5+5) as given in the test cases	Signed arithmetic addition	Verify that output C exactly matches the expected 5-bit result from the golden model
SUBTRACTION	With Opcode = 01, the ALU shall perform signed subtraction (A - B) with correct arithmetic results even for negative operands	Set Opcode to 2'b01 and provide test vectors (0-0, -1-(-1), 4-1) to exercise both zero and nonzero differences	Signed arithmetic subtraction	Check that C equals the computed difference (using two's complement math) for each test vector
INVERT.A	With Opcode = 10, the ALU shall output the bitwise inversion of A with proper sign extension to produce a 5-bit result	Set Opcode to 2'b10 and apply vectors such as A = 4'b0000, 4'b0011, and 4'b1111; B is provided but not used for the inversion operation	Bitwise inversion and sign extension	Confirm that the output C matches the expected sign-extended inversion
REDUCTION.OR.B	With Opcode = 11, the ALU shall perform a reduction OR on B (output 1 if any bit of B is high, otherwise 0), with the result extended to 5 bits	Set Opcode to 2'b11 and stimulate with various values of B (e.g., B = 4'b0000, 4'b1111, 4'b0011) while A can be arbitrary	Reduction logic on B; handling of bitwise reduction operations	Compare the output C with the expected value
DEFAULT.CASE	For undefined or don't care conditions (e.g. Opcode = x or inputs are unknown), the ALU shall output 0, ensuring safe behavior	Drive Opcode and input signals (A, B) to 'x' (unknown) values to check that the default case is properly handled, and that C is driven to 0	Handling of undefined input conditions; safe default outputs	Verify that C is set to 5'b0 when invalid or unknown values are provided

Table 2: Verification Plan

2.3 3. Testbench

```
1 module ALU_4_bit_tb();
2
3     //-----
4     //----- TB signal declaration -----
5     //-----
6     logic clk;
7     logic reset;
8     logic [1:0] Opcode;
9     logic signed [3:0] A, B;
10    logic signed [4:0] C;
11
12    int error_count = 0; // Error count variable
13
14    //-----
15    //----- instantiate DUT -----
16    //-----
17    ALU_4_bit DUT (
18        .clk(clk),
19        .reset(reset),
20        .Opcode(Opcode),
21        .A(A),
22        .B(B),
23        .C(C)
24    );
25
26    //-----
27    //----- generate clock -----
28    //-----
29    localparam CLOCK_PERIOD = 10;
30    always begin
31        #(CLOCK_PERIOD/2) clk = ~clk;
32    end
```

```

33
34 //----- reset task -----
35 //----- reset task -----
36 //----- reset task -----
37 task reset_ALU(input [4:0] expected_output);
38 begin
39     @(posedge clk);
40     if(C != expected_output) begin
41         error_count++;
42         $display("Reset_test_failed: reset=%0b, A=%0b, B=%0b, C=%0b, Opcode=%0b, error_count=%0d, Expected=%0d, time=%0t", reset, A,
43             B, C, Opcode, error_count, expected_output, $time);
44         $stop;
45     end else begin
46         $display("Reset_test_passed: reset=%0b, A=%0b, B=%0b, C=%0b, Opcode=%0b, time=%0t", reset, A, B, C, Opcode, $time);
47         #(CLOCK_PERIOD/2) reset = 0;
48     end
49 end
50 endtask
51
52 //----- test task -----
53 //----- test task -----
54 //----- test task -----
55 task test_ALU(
56     input [1:0] op,
57     input signed [3:0] a,
58     input signed [3:0] b,
59     input signed [4:0] expected_output,
60     input string operation
61 );
62 begin
63     Opcode = op;
64     A = a;
65     B = b;
66     @(posedge clk);
67     #1;
68     if (C != expected_output) begin
69         error_count++;
70         $display("%s_Test_failed: reset=%0b, A=%0b, B=%0b, C=%0b, Opcode=%0b, error_count=%0d, Expected=%0d, Time=%0t",
71             operation, reset, A, B, C, Opcode, error_count, expected_output, $time);
72         $stop;
73     end else begin
74         $display("%s_Test_passed: reset=%0b, A=%0b, B=%0b, C=%0b, Opcode=%0b, Time=%0t",
75             operation, reset, A, B, C, Opcode, $time);
76         #((CLOCK_PERIOD/2)-1);
77     end
78 end
79 end
80 endtask
81
82 //----- initial block -----
83 //----- initial block -----
84 //----- initial block -----
85 initial begin
86     // Initial values
87     clk = 0;
88     reset = 0;
89     Opcode = 2'b01;
90     A = 4'b0100;
91     B = 4'b0011;
92
93     //----- test case 1 : test reset -----
94     //----- test case 1 : test reset -----
95     //----- test case 1 : test reset -----
96     #CLOCK_PERIOD;
97     reset = 1 ;
98     reset_ALU(5'b0);
99
100     //----- test case 2 : test addition -----
101     //----- test case 2 : test addition -----
102     //----- test case 2 : test addition -----
103     test_ALU(2'b00, 4'b0000, 4'b0000, 5'b00000, "Addition"); // Add: 0 + 0 = 0
104     test_ALU(2'b00, 4'b1111, 4'b1111, 5'b11110, "Addition"); // Add: -1 + -1 = -2
105     test_ALU(2'b00, 4'b0011, 4'b0001, 5'b00100, "Addition"); // Add: 3 + 1
106
107     //----- test case 3 : subtraction addition -----
108     //----- test case 3 : subtraction addition -----
109     //----- test case 3 : subtraction addition -----
110     test_ALU(2'b01, 4'b0000, 4'b0000, 5'b00000, "Subtraction"); // Sub: 0 - 0 = 0
111     test_ALU(2'b01, 4'b1111, 4'b1111, 5'b00000, "Subtraction"); // Sub: -1 - -1 = 0
112     test_ALU(2'b01, 4'b0100, 4'b0001, 5'b00011, "Subtraction"); // Sub: 4 - 1 = 3
113
114     //----- test case 4 : invert A "sign extend" -----
115     //----- test case 4 : invert A "sign extend" -----
116     //----- test case 4 : invert A "sign extend" -----
117     test_ALU(2'b10, 4'b0000, 4'b1100, 5'b11111, "Invert_A"); // Not A: ~0 --> 1_1111
118     test_ALU(2'b10, 4'b0011, 4'b0000, 5'b11100, "Invert_A"); // Not A: ~3 --> 1_1100
119     test_ALU(2'b10, 4'b1111, 4'b1111, 5'b00000, "Invert_A"); // Not A: ~-1 --> 0_0000
120
121     //----- test case 5 : Reduction OR B -----
122     //----- test case 5 : Reduction OR B -----
123     //----- test case 5 : Reduction OR B -----
124     test_ALU(2'b11, 4'b1111, 4'b0000, 5'b00000, "Reduction_OR_B"); // Reduction OR B: |0
125     test_ALU(2'b11, 4'b1001, 4'b1111, 5'b00001, "Reduction_OR_B"); // Reduction OR B: |-1
126     test_ALU(2'b11, 4'b0000, 4'b0011, 5'b00001, "Reduction_OR_B"); // Reduction OR B: |3
127
128     // add this bit only fot toggling op code from 11 to 00
129     test_ALU(2'b00, 4'b1011, 4'b0101, 5'b00000, "Addition"); // Add: -5 + 5 = 0
130
131     //----- test case 6 : don't cares "default case" -----
132     //----- test case 6 : don't cares "default case" -----
133     //----- test case 6 : don't cares "default case" -----

```



```
132     test_ALU(2'bxx, 4'bxxxx, 4'bxxxx, 5'b00000, "Default_Case"); // Add: x + x = 0
133
134     // Finish simulation
135     #CLOCK_PERIOD;
136     $finish;
137 end
138
139 endmodule
```

 


Figure 3: simulation waveform

```
*
# Top level modules:
#   ALU_4_bit_tb
# End time: 03:20:47 on Mar 05,2025, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
# vsim -voptargs="+acc" work.ALU_4_bit_tb -coverage
# Start time: 03:20:47 on Mar 05,2025
# ** Note: (vsim-3812) Design is being optimized...
# Loading sv_std.std
# Loading work.ALU_4_bit_tb(fast)
# Loading work.ALU_4_bit(fast)
# Reset test passed: reset=1, A=100, B=11, C=0, Opcode=1, time=15
# Addition Test passed: reset=0, A=0, B=0, C=0, Opcode=0, Time=26
# Addition Test passed: reset=0, A=1111, B=1111, C=11110, Opcode=0, Time=36
# Addition Test passed: reset=0, A=11, B=1, C=100, Opcode=0, Time=46
# Subtraction Test passed: reset=0, A=0, B=0, C=0, Opcode=1, Time=56
# Subtraction Test passed: reset=0, A=1111, B=1111, C=0, Opcode=1, Time=66
# Subtraction Test passed: reset=0, A=100, B=1, C=11, Opcode=1, Time=76
# Invert A Test passed: reset=0, A=0, B=1100, C=11111, Opcode=10, Time=86
# Invert A Test passed: reset=0, A=11, B=0, C=11100, Opcode=10, Time=96
# Invert A Test passed: reset=0, A=1111, B=1111, C=0, Opcode=10, Time=106
# Reduction OR B Test passed: reset=0, A=1111, B=0, C=0, Opcode=11, Time=116
# Reduction OR B Test passed: reset=0, A=1001, B=1111, C=1, Opcode=11, Time=126
# Reduction OR B Test passed: reset=0, A=0, B=11, C=1, Opcode=11, Time=136
# Addition Test passed: reset=0, A=1011, B=101, C=0, Opcode=0, Time=146
# Default Case Test passed: reset=0, A=x, B=x, C=0, Opcode=x, Time=156
# ** Note: $finish : ALU_4_bit_tb.sv(139)
#   Time: 170 ns  Iteration: 0  Instance: /ALU_4_bit_tb
# 1
# Break in Module ALU_4_bit_tb at ALU_4_bit_tb.sv line 139
```

Figure 4: Transcript : all test cases passed

2.4 4. Do File

```
vlib work
vlog ALU_4_bit.sv ALU_4_bit_tb.sv +cover -covercells
vsim -voptargs="+acc" work.ALU_4_bit_tb -cover
add wave *
coverage save ALU_4_bit_tb.ucdb -du ALU_4.bit -onexit
run -all
```

2.5 5. Coverage Report

Coverage Report by instance with details

Instance: /\ALU_4_bit_tb#DUT				
Design Unit: work.ALU_4_bit				
Branch Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Branches	7	7	0	100.00%
Branch Details				
Branch Coverage for instance /\ALU_4_bit_tb#DUT				
Line	Item	Count	Source	
File	ALU_4_bit.sv			
CASE Branch				
21		15	Count coming in to CASE	
22	1	4	Add:	A + B
23	1	4	Sub:	A - B
24	1	3	Not_A:	~A
25	1	3	ReductionOR_B:	A   B
26	1	1	default:	Alu_out = 5'b0
Branch totals: 5 hits of 5 branches = 100.00%				
IF Branch				



32		17	Count coming in to IF
32	1	2	if (reset)
34	1	15	else

Branch totals: 2 hits of 2 branches = 100.00%

Statement Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Statements	9	9	0	100.00%

Statement Details

Statement Coverage for instance /\ALU\_4\_bit\_tb#DUT —

Line	Item	Count	Source
File	ALU_4_bit.sv		
1			module ALU_4_bit (
2			input clk ,
3			input reset ,
4			input [1:0] Opcode, // The opcode
5			input signed [3:0] A, // Input data A in 2's complement
6			input signed [3:0] B, // Input data B in 2's complement
7			
8			output reg signed [4:0] C // ALU output in 2's complement
9			
10			);
11			
12			reg signed [4:0] Alu_out; // ALU output in 2's complement
13			
14			localparam Add = 2'b00; // A + B
15			localparam Sub = 2'b01; // A - B
16			localparam Not_A = 2'b10; // ~A
17			localparam ReductionOR_B = 2'b11; //  B
18			
19			// Do the operation
20	1	15	always @* begin
21			case (Opcode)
22	1	4	Add: Alu_out = A + B;
23	1	4	Sub: Alu_out = A - B;
24	1	3	Not_A: Alu_out = ~A;
25	1	3	ReductionOR_B: Alu_out =  B;
26	1	1	default:
27			endcase
28			end // always @ *
29			
30			// Register output C
31	1	17	always @(posedge clk or posedge reset) begin
32			if (reset)
33	1	2	C <= 5'b0;
34			else
35	1	15	C<= Alu_out;

Toggle Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Toggles	44	44	0	100.00%

Toggle Details

Toggle Coverage for instance /\ALU\_4\_bit\_tb#DUT —

	Node	1H→0L	0L→1H	" Coverage"
	A[0–3]	1	1	100.00
	Alu_out[4–0]	1	1	100.00
	B[0–3]	1	1	100.00
	C[4–0]	1	1	100.00
	Opcode[0–1]	1	1	100.00
	clk	1	1	100.00
	reset	1	1	100.00

Total Node Count	=	22
Toggled Node Count	=	22
Untoggled Node Count	=	0

Toggle Coverage = 100.00% (44 of 44 bins)

Total Coverage By Instance (filtered view): 100.00%

### 3 DSP

#### 3.1 1 Design

```

1 module DSP(A, B, C, D, clk, rst_n, P);
2   parameter OPERATION = "ADD";
3   input  [17:0] A, B, D;
4   input  [47:0] C;
5   input  clk, rst_n;
6   output reg  [47:0] P;

```

```
7
8 reg [17:0] A_reg_stg1, A_reg_stg2, B_reg, D_reg;
9 reg [18:0] adder_out_stg1, adder_out_stg2;
10 reg [47:0] C_reg;
11 reg [36:0] mult_out;
12
13 always @(posedge clk or negedge rst_n) begin
14     if (!rst_n) begin
15         // reset
16         A_reg_stg1 <= 0;
17         A_reg_stg2 <= 0;
18         B_reg <= 0;
19         D_reg <= 0;
20         C_reg <= 0;
21         adder_out_stg1 <= 0;
22         adder_out_stg2 <= 0;
23         mult_out <= 0;
24         P <= 0;
25     end
26     else begin
27         A_reg_stg1 <= A;
28         A_reg_stg2 <= A_reg_stg1;
29         B_reg <= B;
30         C_reg <= C;
31         D_reg <= D;
32         adder_out_stg2 <= adder_out_stg1;
33         if (OPERATION == "ADD") begin
34             adder_out_stg1 <= D_reg + B_reg;
35             P <= mult_out + C_reg;
36         end
37         else if (OPERATION == "SUBTRACT") begin
38             adder_out_stg1 <= D_reg - B_reg;
39             P <= {{11{mult_out[36]}},mult_out} - C_reg;
40         end
41         mult_out <= A_reg_stg2 * adder_out_stg2;
42     end
43 end
44
45 endmodule
```

3.2 Bug Fixes

- **Bug 1: Adder Output Width Mismatch**
  - Issue: The adder output was stored in 18-bit registers Since the sum or difference of two 18-bit inputs (D\_reg + B\_reg or D\_reg - B\_reg) can produce a 19-bit result, this caused overflow and data truncation.
  - Fix: Increased the adder output width to 19 bits
- **Bug 2: Multiplier Output Width Mismatch**
  - Issue: The multiplier output was defined as 48 bits However, multiplying two 18-bit numbers (A\_reg\_stg2 \* adder\_out\_stg2) produces a maximum of a 36-bit result, leading to an over-provisioned width and potential misalignment in subsequent operations
  - Fix: Adjusted to 37 bits
- **Bug 3: Sign Extension Error**
  - Issue: The subtraction operation did not properly account for the width mismatch between the 37-bit multiplier output (mult\_out) and the 48-bit accumulation register (P). This could cause incorrect behavior due to the absence of sign extension
  - Fix: Sign extension was added to mult\_out before the subtraction, ensuring proper 48-bit alignment
- **Bug 4: Uninitialized Registers**
  - Issue: The following registers did not have an initial reset value, leading to potential X (unknown) states during simulation or invalid values during hardware power-up: [ adder\_out\_stg2 & C\_reg ]
  - Fix: Added reset logic for all registers

3.3 2. Verification Plan

Label	Design Requirement Description	Stimulus Generation	Functional Coverage	Functionality Check
RESET.TEST	When reset is asserted, the output P should be zero	Directed at the start of the simulation	-	A checker verifies P == 0 during reset
ADD.TEST	Perform ADD operation: P = (A * (D + B)) + C	Randomized inputs	-	Compare P to golden model result
SUB.TEST	Perform SUBTRACT operation: P = (A * (D - B)) - C	Randomized inputs	-	Compare P to golden model result
RAND.TEST	Randomize A, B, C, D inputs and verify correct ADD/SUBTRACT results	Randomization with constraints	-	Verify against golden model

Table 3: Verification Plan

3.4 3 Testbench

```
1 module DSP_tb;
2     //-----
3     // Declare signals
4     //-----
5     reg [17:0] A, B, D;
6     reg [47:0] C;
7     reg clk, rst_n;
8     wire [47:0] P;
9
10    //-----
11    // Instantiate the DUT (Device Under Test)
12    //-----
13    DSP #(.OPERATION("ADD")) dut (
14        .A(A),
15        .B(B),
```

```

16         .C(C),
17         .D(D),
18         .clk(clk),
19         .rst_n(rst_n),
20         .P(P)
21     );
22
23     //-----
24     // Golden Model
25     //-----
26     reg [47:0] golden_P;
27
28     //-----
29     // Clock generation
30     //-----
31     parameter CLOCK_PERIOD = 10;
32     always begin
33         #(CLOCK_PERIOD/2) clk = ~clk;
34     end
35
36     //-----
37     // Reset task
38     //-----
39     task reset_dut;
40     begin
41         // Assert reset
42         rst_n = 0;
43         @(posedge clk);
44
45         // Check output reset to zero
46         if (P != 48'b0) begin
47             $display("Reset_test_failed: rst_n=%0b, A=%0d, B=%0d, D=%0d, C=%0d, P=%0d", rst_n, A, B, D, C, P);
48             $stop;
49         end else begin
50             $display("Reset_test_passed: rst_n=%0b, A=%0d, B=%0d, D=%0d, C=%0d, P=%0d", rst_n, A, B, D, C, P);
51         end
52
53         // Deassert reset
54         #(CLOCK_PERIOD/2);
55         rst_n = 1;
56     end
57 endtask
58
59 //-----
60 // Check "ADD" result task
61 //-----
62 task check_ADD_result;
63 begin
64     // Golden model calculation
65     golden_P = (A * (D + B)) + C;
66
67     // Wait for 4 clock cycles
68     #50;
69
70     // Compare the output with the golden model
71     if (P != golden_P) begin
72         $display("Error: in ADD_TEST Mismatch found! Expected: %h, Got: %h, rst_n=%0b, A=%0h, B=%0h, D=%0h, C=%0h", golden_P,
73             P, rst_n, A, B, D, C);
74         $stop;
75     end else begin
76         $display("Success: in ADD_TEST Output matches the golden model. P=%d, rst_n=%0b, A=%0h, B=%0h, D=%0h, C=%0h", P,
77             rst_n, A, B, D, C);
78     end
79 end
80 endtask
81
82 //-----
83 // Check "SUBTRACT" result task
84 //-----
85 task check_sub_result;
86 begin
87     // Golden model calculation
88     golden_P = (A[17:0] * (D [17:0] - B[17:0])) - C;
89
90     // Wait for 4 clock cycles
91     #50;
92
93     // Compare the output with the golden model
94     if (P != golden_P) begin
95         $display("Error: in sub_TEST Mismatch found! Expected: %h, Got: %h, rst_n=%0b, A=%0h, B=%0h, D=%0h, C=%0h", golden_P,
96             P, rst_n, A, B, D, C);
97         $stop;
98     end else begin
99         $display("Success: in sub_TEST Output matches the golden model. P=%d, rst_n=%0b, A=%0h, B=%0h, D=%0h, C=%0h", P,
100             rst_n, A, B, D, C);
101     end
102 end
103 endtask
104
105 //-----
106 // Randomization with constraints
107 //-----
108 class InputValues;
109 rand reg [17:0] A, B, D;
110 rand reg [47:0] C;
111
112 // Balanced distribution for extreme and mid-range values
113 constraint balanced_values {
114     A dist { 18'h00000 := 10, 18'h3FFFF := 40, [18'h00001:18'h3FFFE] :/ 50 };
115     B dist { 18'h00000 := 10, 18'h3FFFF := 40, [18'h00001:18'h3FFFE] :/ 50 };

```

```
112     D dist { 18'h00000 := 10, 18'h3FFFF := 40, [18'h00001:18'h3FFFE] :/ 50 };
113     C dist { 48'h0000000000000 := 10, 48'hFFFFFFFFFFFF := 40, [48'h0000000000001:48'hFFFFFFFFFFFFE] :/ 50 };
114 }
115 endclass
116
117
118 InputValues inputs;
119
120 //-----
121 // Randomization and simulation procedure.
122 //-----
123 initial begin
124     //-----
125     // Initialize signals
126     //-----
127     clk = 1'b0;
128     rst_n = 1'b1;
129     A = 1;
130 B = 4;
131 C = 2;
132 D = 16;
133
134     #(CLOCK_PERIOD);
135
136     //-----
137     // Check reset functionality
138     //-----
139     reset_dut;
140
141     //-----
142     // Start the test
143     //-----
144     inputs = new();
145     for (int i = 0; i < 20; i = i + 1) begin
146         if (inputs.randomize()) begin
147             A = inputs.A;
148             B = inputs.B;
149             C = inputs.C;
150             D = inputs.D;
151         end else begin
152             $display("Randomization failed.");
153             $stop;
154         end
155
156         // Call the check ADD result task
157         // operation = "ADD";
158         check_ADD_result;
159
160         // Call the check subtract result task
161         // operation = "SUBTRACT";
162         // check_sub_result;
163     end
164
165     // Finish the simulation
166     $finish;
167 end
168 endmodule
```

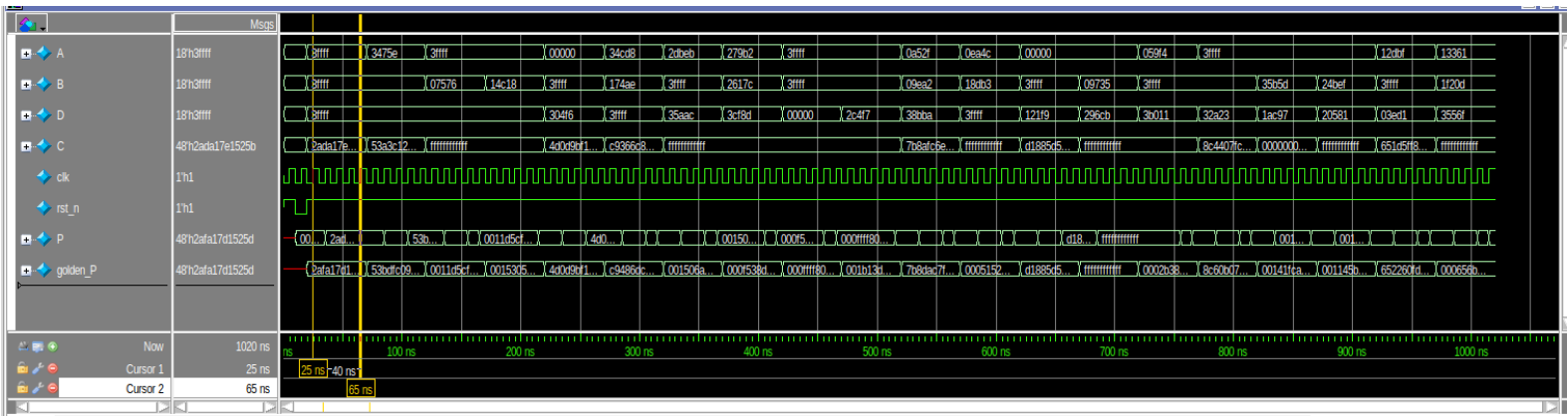


Figure 5: simulation wave form

```

# Saving coverage database on exit...
# End time: 07:39:02 on Mar 06,2025, Elapsed time: 0:02:03
# Errors: 0, Warnings: 0
# vsim -voptargs="+acc" DSP_tb -coverage
# Start time: 07:39:02 on Mar 06,2025
# ** Note: (vsim-8009) Loading existing optimized design_opt
# Loading sv_std.std
# Loading work.DSP_tb(fast)
# Loading work.DSP(fast)
# Reset test passed: rst_n=0 , A=1 , B=4 , D=16 , C=2 , P=0
# Success: in ADD TEST Output matches the golden model. P = 47253629784669 ,rst_n=1 , A=3ffff , B=3ffff , D=3ffff , C=2adal7e1525b
# Success: in ADD TEST Output matches the golden model. P = 92075442417557 ,rst_n=1 , A=3475e , B=3ffff , D=3ffff , C=53a3c1203e51
# Success: in ADD TEST Output matches the golden model. P = 76601592458 ,rst_n=1 , A=3ffff , B=7576 , D=3ffff , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 91005301736 ,rst_n=1 , A=3ffff , B=14c18 , D=3ffff , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 84720846239339 ,rst_n=1 , A=0 , B=3ffff , D=304f6 , C=4d0d9b1f666b
# Success: in ADD TEST Output matches the golden model. P = 221312916716308 ,rst_n=1 , A=34cd8 , B=174ae , D=3ffff , C=c9366c842dlc
# Success: in ADD TEST Output matches the golden model. P = 90305889272 ,rst_n=1 , A=2dbeb , B=3ffff , D=35aac , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 65826281793 ,rst_n=1 , A=279b2 , B=2617c , D=3cf8d , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 68718952448 ,rst_n=1 , A=3ffff , B=3ffff , D=0 , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 116296596233 ,rst_n=1 , A=3ffff , B=3ffff , D=2c4f7 , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 135848414647937 ,rst_n=1 , A=a52f , B=9ea2 , D=38bba , C=7b8afc6e839d
# Success: in ADD TEST Output matches the golden model. P = 21829960919 ,rst_n=1 , A=ea4c , B=18db3 , D=3ffff , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 230383611827441 ,rst_n=1 , A=0 , B=3ffff , D=121f9 , C=d1885d5854f1
# Success: in ADD TEST Output matches the golden model. P = 281474976710655 ,rst_n=1 , A=0 , B=9735 , D=296cb , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 11602059071 ,rst_n=1 , A=59f4 , B=3ffff , D=3b011 , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 154346905733293 ,rst_n=1 , A=3ffff , B=3ffff , D=32a23 , C=8c4407fc32cf
# Success: in ADD TEST Output matches the golden model. P = 86432741388 ,rst_n=1 , A=3ffff , B=35b5d , D=1ac97 , C=0
# Success: in ADD TEST Output matches the golden model. P = 74184371855 ,rst_n=1 , A=3ffff , B=24bef , D=20581 , C=fffffffffffff
# Success: in ADD TEST Output matches the golden model. P = 111198330549450 ,rst_n=1 , A=12dbf , B=3ffff , D=3ed1 , C=651d5ff8879a
# Success: in ADD TEST Output matches the golden model. P = 27224820219 ,rst_n=1 , A=13361 , B=1f20d , D=3556f , C=fffffffffffff
# ** Note: $finish : DSP_tb.sv(166)
# Time: 1020 ns Iteration: 0 Instance: /DSP_tb
# 1

```

Figure 6: transcript : all tests passed

### 3.5 4 Do File

```

vlib work
vlog DSP.v DSP_tb.sv +cover -covercells
vsim -voptargs="+acc" DSP_tb -cover
add wave *
coverage save DSP_tb.ucdb -du DSP -onexit
run -all

```

### 3.6 5 Coverage Report

Coverage Report by instance with details

Instance: /\DSP_tb#dut				
Design Unit: work.DSP				
Branch Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Branches	2	2	0	100.00%
Branch Details				
Branch Coverage for instance /\DSP_tb#dut				
Line	Item	Count	Source	
File DSP.v				
IF Branch				
14		102	Count coming in to IF	
14	1	2	if (!rst_n) begin	
26	1	100	else begin	
Branch totals: 2 hits of 2 branches = 100.00%				
Statement Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Statements	19	19	0	100.00%
Statement Details				
Statement Coverage for instance /\DSP_tb#dut				
Line	Item	Count	Source	
File DSP.v				
1			module DSP(A, B, C, D, clk , rst_n , P);	
2			parameter OPERATION = "ADD";	
3			input [17:0] A, B, D;	
4			input [47:0] C;	
5			input clk , rst_n;	
6			output reg [47:0] P;	
7				
8			reg [17:0] A_reg_stg1 , A_reg_stg2 , B_reg , D_reg;	
9			reg [18:0] adder_out_stg1 , adder_out_stg2;	
10			reg [47:0] C_reg;	
11			reg [36:0] mult_out;	
12				
13	1	102	always @(posedge clk or negedge rst_n) begin	
14			if (!rst_n) begin	
15			// reset	
16	1	2	A_reg_stg1 <= 0;	
17	1	2	A_reg_stg2 <= 0;	

18	1	2	B_reg <= 0;
19	1	2	D_reg <= 0;
20	1	2	C_reg <= 0;
21	1	2	adder_out_stg1 <= 0;
22	1	2	adder_out_stg2 <= 0;
23	1	2	mult_out <= 0;
24	1	2	P <= 0;
25			end
26			else begin
27	1	100	A_reg_stg1 <= A;
28	1	100	A_reg_stg2 <= A_reg_stg1;
29	1	100	B_reg <= B;
30	1	100	C_reg <= C;
31	1	100	D_reg <= D;
32	1	100	adder_out_stg2 <= adder_out_stg1;
33			if (OPERATION == "ADD") begin
34	1	100	adder_out_stg1 <= D_reg + B_reg;
35	1	100	P <= mult_out + C_reg;
36			end
37			else if (OPERATION == "SUBTRACT") begin
38			adder_out_stg1 <= D_reg - B_reg;
39			P <= {{11{mult_out[36]}} , mult_out} - C_reg;
40			end
41	1	100	mult_out <= A_reg_stg2 * adder_out_stg2;

Toggle Coverage:				
Enabled Coverage	Bins	Hits	Misses	Coverage
Toggles	694	694	0	100.00%

=====Toggle Details=====

Toggle Coverage for instance /\DSP\_tb#dut —

	Node	1H→0L	0L→1H	" Coverage"
	A[0–17]	1	1	100.00
	A_reg_stg1[17–0]	1	1	100.00
	A_reg_stg2[17–0]	1	1	100.00
	B[0–17]	1	1	100.00
	B_reg[17–0]	1	1	100.00
	C[0–47]	1	1	100.00
	C_reg[47–0]	1	1	100.00
	D[0–17]	1	1	100.00
	D_reg[17–0]	1	1	100.00
	P[47–0]	1	1	100.00
	adder_out_stg1[18–0]	1	1	100.00
	adder_out_stg2[18–0]	1	1	100.00
	clk	1	1	100.00
	mult_out[36–0]	1	1	100.00
	rst_n	1	1	100.00

Total Node Count	=	347
Toggled Node Count	=	347
Untoggled Node Count	=	0
Toggle Coverage	=	100.00% (694 of 694 bins)

Total Coverage By Instance (filtered view): 100.00%